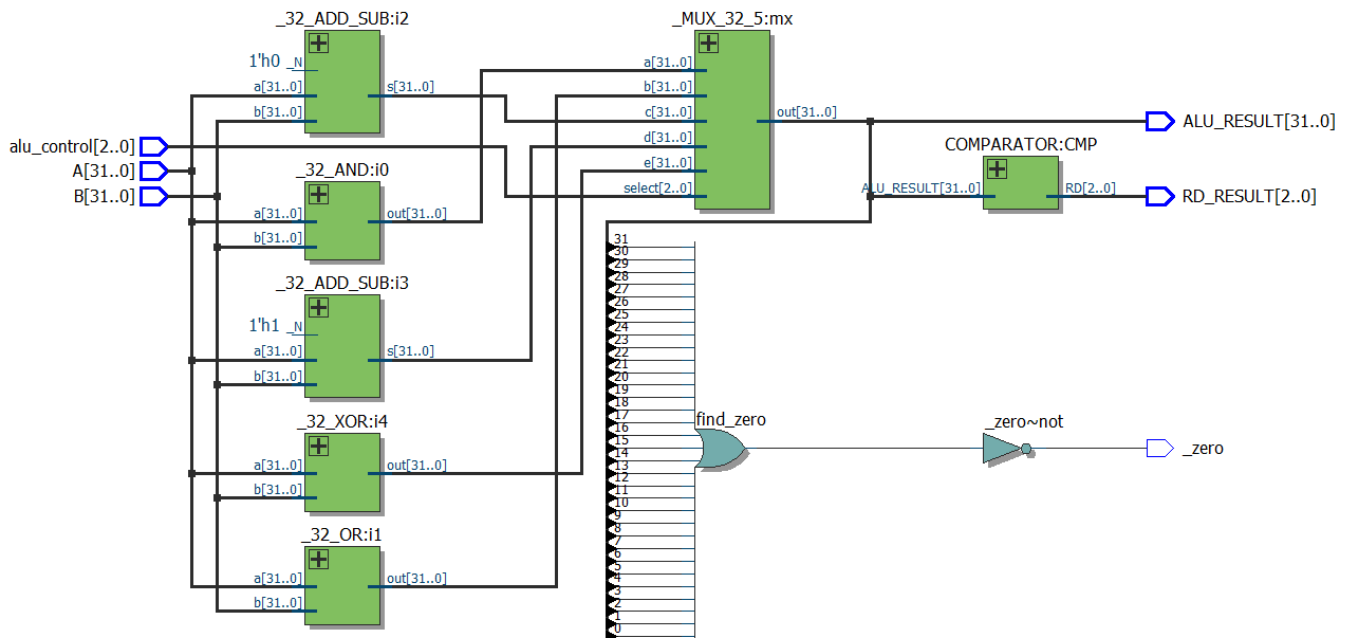



ALU 32 MODULE TEST RESULT (for ALU RESULT as \$RS[op]\$RT):

```
# ==> ORN  :: A = 11111111111111111111111111111111, B = 00000000000000000000000000000001, SEL=000, RESULT=00000000000000000000000000000001
# ==> ADDN :: A = 11111111111111111111111111111111, B = 00000000000000000000000000000001, SEL=001, RESULT=11111111111111111111111111111111
# ==> SUBN :: A = 01000000000111010110000000000001, B = 0111110000000000000000011100000100, SEL=010, RESULT=101111000000111010110011100000101
# ==> XORN :: A = 11111111111111111111111111111111, B = 00000000000000000000000000000000, SEL=011, RESULT=11111111111111111111111111111111
```

RTL VIEW OF ALU WITH COMPARATOR:




RTL VIEW OF COMPARATOR:

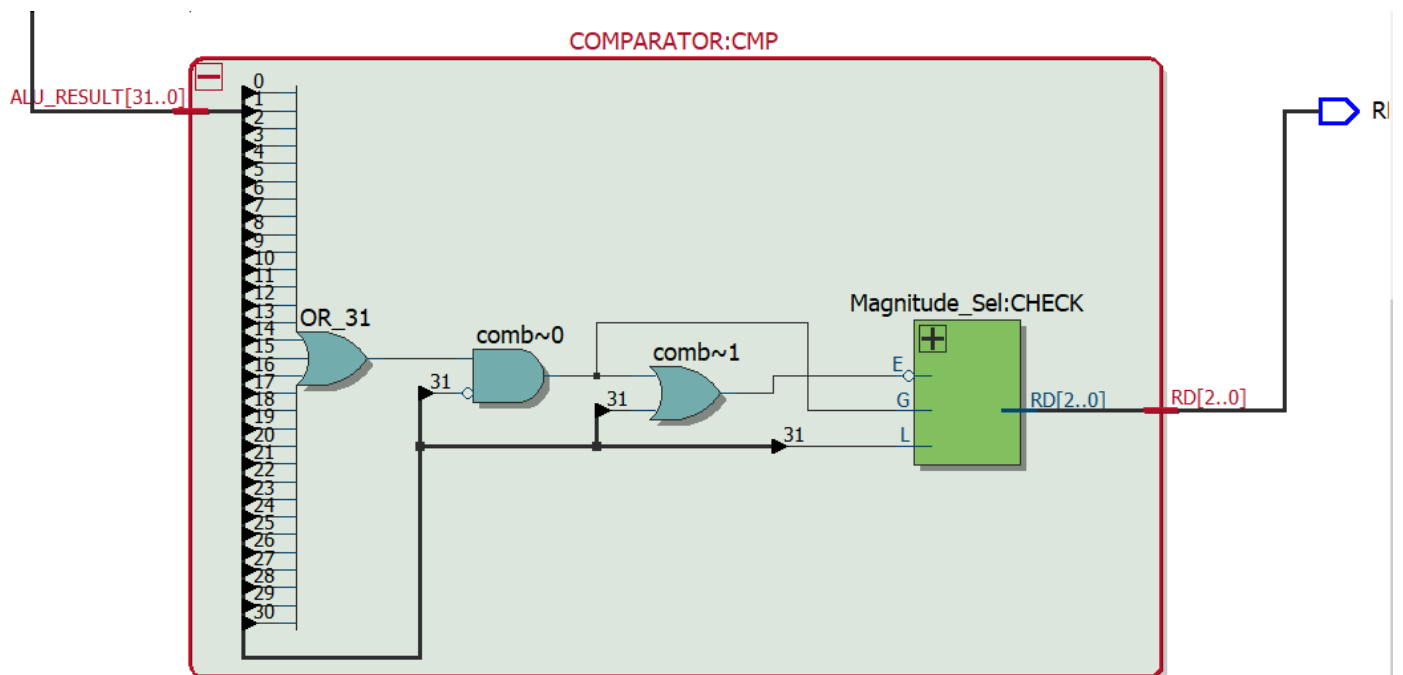


ALU 32 MODULE TEST RESULT (RD RESULT AFTER COMPARATOR):

[illegible][illegible]

RTL VIEW OF ALU CONTROL:

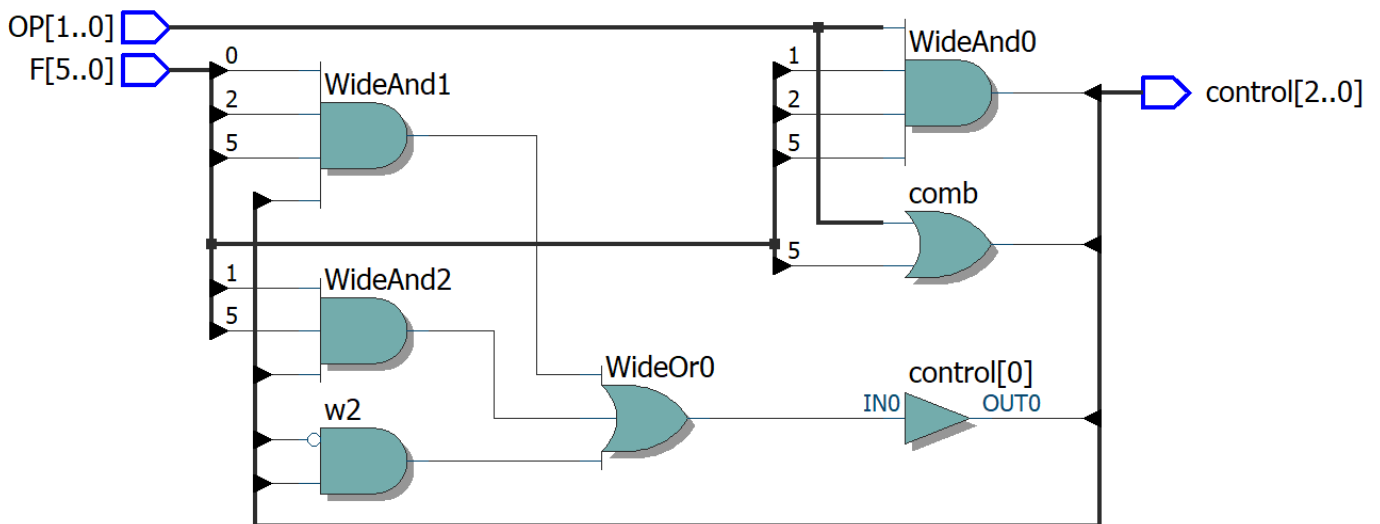

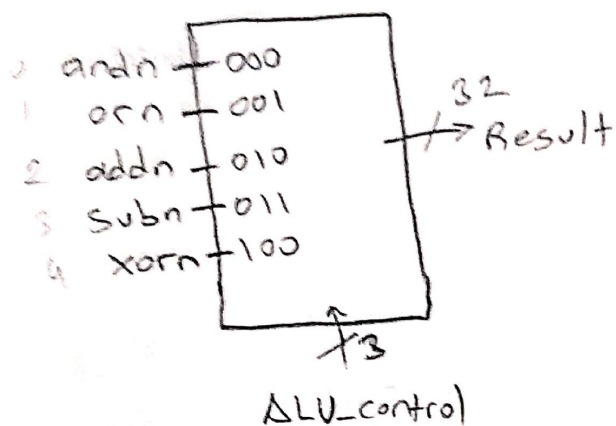


ALU-control:

[2] =

[1] =

[0] =

 

Comparator

$rs + rt = \text{ALU-Result}$


if $(rs + rt == 0)$ $\$rd \leftarrow 1$

else if $(rs + rt < 0)$ $\$rd \leftarrow 2$

else $\$rd \leftarrow 3$

• ALU module has a RD-RESULT output.

new ALU →

 


lw	00	X	010
sw	00	X	010
beq	01	X	011
andn	10	100100	000
orn	10	100101	001
addn	10	100000	010
subn	10	100010	011
xorn	10	100110	100
	ALU op [1-0]	function [5-0]	ALU control

$$\text{Control}[2] = \text{ALUop1} \cdot F5 \cdot F2 \cdot F1$$

$$\text{Control}[1] = \text{ALUop1} + F5$$
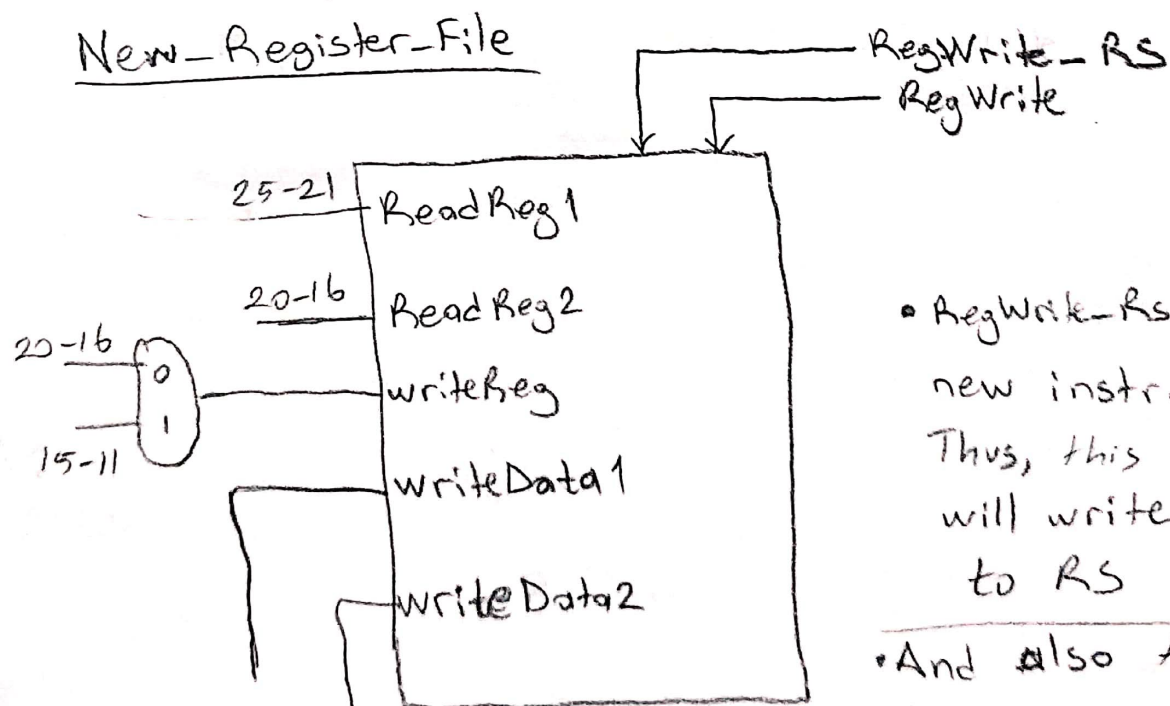
$$\text{Control}[0] = \overline{\text{ALUop1}} \cdot \text{ALUop0} + \text{ALUop1} \cdot F5 \cdot F2 \cdot F0 + \text{ALUop1} \cdot F5 \cdot F1$$




• RegWrite-RS means new instructions. Thus, this command will write data to RS

• And also to write RS, instruction mux should be $\text{RD}[15-11]$

They will be written at the same clock time (RS, RD)

mips-register module

 

**NOTE : I COULD NOT MADE THE DATAPATH CONNECTIONS PROPERLY
THEREFORE I SUBMIT ONLY MODULES THAT I MADE.**

I HAVE THE FOLLOWING MAIN MODULES IN MY ASSIGNMENT:

```

module _HA(s, c, a, b);
module _FA(sum, carry_out, a, b, carry_in);
module _32_AND (out, a, b);
module _32_OR (out, a, b);
module _32_NOR (out, a, b);
module _32_XOR (out, a, b);
module _32_ADD_SUB (s,a,b,_N);
`define DELAY 50
module _32_ADD_SUB_testbench();

```

```

//=====
module _MUX_2_1 (out,a,b, select);
//=====
module _MUX_32_4 (out, a,b,c,d, select0, select1);
//=====
module _MUX_32_8 (out, a,b,c,d,e,f,g,h, select);
//=====
module _MUX_32_2 (out,a,b, select);
//=====
module _MUX_32_5 (out, a,b,c,d,e, select);
//=====

```

```

... module _PC (clock,jump_signal,beq_signal,beq_equal,extended_32); ...
endmodule
... module Next_PC (nextPC,clock,jump_signal,branch_signal,CurrentPC); ...
endmodule
...

```

```

module mips_registers( read_data_1, read_data_2,
                      write_data1,write_data2,
                      read_reg_1, read_reg_2,
                      write_reg, reg_write_signal,
                      reg_write_RS_signal,clk);

```

```

module ALU_32 (ALU_RESULT, A, B, alu_control, RD_RESULT, _zero);
  input [31:0] A, B;
  input [2:0] alu_control;
  output [31:0] ALU_RESULT;
  output [2:0] RD_RESULT;
  output _zero;

```

```

`define DELAY 50
module ALU_32_testbench();
  reg [31:0]a, b;
  reg [2:0]alu_cntrol;
  wire [31:0] alu_result;
  wire [2:0] RD;
  wire _zero;
  ALU_32 alu(alu_result, a, b, alu_cntrol, RD, _zero);
  initial begin

```

```

module ALU_CONTROL (input [5:0] F, input [1:0] OP, output [2:0] control);

wire w1,w2,w3,w4;

and ( control[2], OP[1],F[5],F[2],F[1] );
or ( control[1], OP[1],F[5] );
not (w1,control[1]);
and (w2,w1,control[0]);
and (w3,control[1],F[5],F[2],F[0] );
and (w4,control[1],F[5],F[1]);
or ( control[0], w2, w3, w4);

endmodule

```

```

... module COMPARATOR ( input [31:0] ALU_RESULT, output [2:0] RD ); ...
endmodule

```

```

...
module COMPARATOR_tb; ...

```

```

module Magnitude_Sel ( G,E,L, RD ); ...
...
... endmodule

... module Magnitude_Sel_TB(); ...
...
endmodule

```

```

module data_mem (read_data, mem_address, write_data, memRead_signal, signal_memWrite,clock);
    output reg [31:0] read_data;
    input [31:0] mem_address,write_data;
    input memRead_signal,signal_memWrite,clock;

```

```

module instr_mem(instruction ,PC);
    input [31:0] PC;
    output reg [31:0] instruction;
    reg [31:0] instr_mem [255:0];
    //always takes the instruction with PC
    always @(*) begin
        instruction = instr_mem[PC];
    end
endmodule

```

```

module jump_address(jump_address,instr,PC,zero);
    input[3:0] PC;
    input zero;
    input [25:0]instr;
    output[31:0]jump_address;

```

```

module zero_extend(_imm,zeroExt_imm,zero);
    input [15:0] _imm;
    input zero;
    output [31:0] zeroExt_imm;

```

```

module sign_extend_imm(_imm,signExt_imm);
    input [15:0] _imm;
    output [31:0] signExt_imm;

```

The data memory size will be 256KB whereas the instruction memory size will be 16KB. Remember that addressing for a 256KB memory only requires 18 bits instead of 32 bits in regular MIPS. Update your design accordingly.

NOTE : I encountered some problems when working with 18 bit instead of 32 thus I made connections as 32 bit in memory modules.